
# Linear Bounds on Circuit Complexity and Feebly One-way Permutations

Grigory Yaroslavtsev

Academic University, Saint-Petersburg, Russia http://logic.pdmi.ras.ru/~grigory

April 5, 2010

### Plan

 

- 2 Upper bounds on circuit complexity
- 3 Lower bounds on circuit complexity



Feebly one-way families of permutations

### Motivation

Practical:

• Logical design synthesis: smaller circuits — better designs.

### Motivation

Practical:


• Logical design synthesis: smaller circuits — better designs.

Theoretical:

• Circuits — very simple and natural model of computation. Many efforts spent — not too much known.
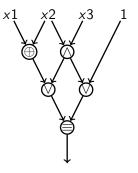
### **Boolean Circuits**

- inputs: propositional variables  $x_1, x_2, \dots, x_n$  and constants 0, 1
- gates: binary functions
- fan-out of a gate is unbounded



# Symmetric functions

#### Definition

A boolean function is symmetric if its value depends on the sum of the input values only.

Example:  $MAJ(x_1, \ldots, x_n) = 1 \iff x_1 + \ldots + x_n \ge n/2$ 

# Symmetric functions

### Definition

A boolean function is symmetric if its value depends on the sum of the input values only.

Example: 
$$MAJ(x_1, \ldots, x_n) = 1 \iff x_1 + \ldots + x_n \ge n/2$$

#### Modular functions

Let  $MOD_{m,r}^n(x_1,\ldots,x_n) = 1 \iff \sum_{i=1}^n x_i \equiv r \pmod{m}$ .

Example: MOD<sup>n</sup><sub>4,0</sub>( $x_1, \ldots, x_n = 1$ )  $\iff \sum_{i=1}^n x_i \equiv \{0, 4, 8, \ldots\}$ 

# Stockmeyer's bounds for $MOD_{4,0}^n$

• Stockmeyer constructed a circuit for  $MOD_{4,0}^n$  of size 2.5n + c, using blocks with 6 inputs and 10 gates to add 4 new values to the remainder encoded by 2 bits and transfer the remainder encoded in 2 bits to the next block.

# Stockmeyer's bounds for $MOD_{4,0}^n$

- Stockmeyer constructed a circuit for  $MOD_{4,0}^n$  of size 2.5n + c, using blocks with 6 inputs and 10 gates to add 4 new values to the remainder encoded by 2 bits and transfer the remainder encoded in 2 bits to the next block.
- This matches the corresponding lower bound 2.5n + c proved by him.

# Applying practice to theory

"For many important functions there is a large gap between known lower and upper bounds. It might be helpful to know optimal circuits for such functions at least for small values of input size. Knowing this could help us to understand the structure of optimal circuits for general functions."

Williams, R. (2008)

# Applying practice to theory

"For many important functions there is a large gap between known lower and upper bounds. It might be helpful to know optimal circuits for such functions at least for small values of input size. Knowing this could help us to understand the structure of optimal circuits for general functions."

Williams, R. (2008)

By finding efficient small circuits we can obtain upper bounds on circuit complexity.

### Bruteforce search

 The number F(n, t) of circuits of size ≤ t with n input variables does not exceed

$$\left(16(t+n+2)^2\right)^t\,.$$

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variable or a constant ( $\leq n + 2$  choices).

### Bruteforce search

 The number F(n, t) of circuits of size ≤ t with n input variables does not exceed

$$\left(16(t+n+2)^2\right)^t$$
.

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variable or a constant ( $\leq n + 2$  choices).

• To find Stockmeyer's block (6 inputs, 10 gates) a naive bruteforce over  $\sim 1.4*10^{37}$  circuits will be needed.

Given a function  $f : \{0,1\}^n \to \{0,1\}^m$  (n, m are constants) we transform the fact "there exists a circuit of size m computing function f" into a CNF formula and use SAT-solvers to check its satisfiability.

Given a function  $f : \{0,1\}^n \to \{0,1\}^m$  (n, m are constants) we transform the fact "there exists a circuit of size m computing function f" into a CNF formula and use SAT-solvers to check its satisfiability.

### Enconding

- All possible underlying graphs of circuit
- All possibilities for functions computed by gates
- Which gates are outputs
- The particular function computed by circuit

### Results

#### Results

• New upper bound for  $MOD_{3,*}^n$ : 3n + c in full binary basis  $B_2$  (previous 5n + c), using a block with 5 inputs and 9 gates.

### Results

#### Results

- New upper bound for  $MOD_{3,*}^n$ : 3n + c in full binary basis  $B_2$  (previous 5n + c), using a block with 5 inputs and 9 gates.
- New upper bound for  $MOD_{3,*}^n$ : 5.5n + c in basis  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  (previous 7n + c), using a block with 4 inputs and 11 gates.

### Results

#### Results

- New upper bound for  $MOD_{3,*}^n$ : 3n + c in full binary basis  $B_2$  (previous 5n + c), using a block with 5 inputs and 9 gates.
- New upper bound for  $MOD_{3,*}^n$ : 5.5n + c in basis  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  (previous 7n + c), using a block with 4 inputs and 11 gates.
- It is possible to prove exact bounds for circuits with  $\leq$  8 gates.

• Shannon counting argument: count how many different Boolean functions in *n* variables can be computed by circuits with *t* gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.

- Shannon counting argument: count how many different Boolean functions in *n* variables can be computed by circuits with *t* gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number F(n, t) of circuits of size ≤ t with n input variables does not exceed

 $\left(16(t+n+2)^2\right)^t.$ 

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variables or a constant ( $\leq n + 2$  choices).

- Shannon counting argument: count how many different Boolean functions in *n* variables can be computed by circuits with *t* gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number F(n, t) of circuits of size ≤ t with n input variables does not exceed

 $\left(16(t+n+2)^2\right)^t.$ 

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variables or a constant ( $\leq n + 2$  choices).

• For  $t = 2^n/(10n)$ , F(n, t) is approximately  $2^{2^n/5}$ , which is  $\ll 2^{2^n}$ .

- Shannon counting argument: count how many different Boolean functions in *n* variables can be computed by circuits with *t* gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number F(n, t) of circuits of size ≤ t with n input variables does not exceed

 $\left(16(t+n+2)^2\right)^t.$ 

Each of t gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variables or a constant ( $\leq n + 2$  choices).

• For  $t = 2^n/(10n)$ , F(n, t) is approximately  $2^{2^n/5}$ , which is  $\ll 2^{2^n}$ .

• Thus, the circuit complexity of almost all Boolean functions on *n* variables is exponential in *n*. Still, we do not know any explicit function with super-linear circuit complexity.

Grigory Yaroslavtsev (SPb AU)

# Known Lower Bounds

	circuit size	formula size
full binary basis $B_2$	3n-o(n)	$n^{2-o(1)}$
	[Blum]	[Nechiporuk]
basis $U_2 = B_2 \setminus \{\oplus, \equiv\}$	5n-o(n)	$n^{3-o(1)}$
	[lwama et al.]	[Hastad]
	exponential	
monotone basis $M_2 = \{\lor, \land\}$	[Razborov; Alon, Boppana;	
	Andreev; Karchmer, Wigderson]	

• We are interested in explicitly defined Boolean functions of high circuit complexity.

- We are interested in explicitly defined Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on *n* variables and take the first with circuit complexity at least  $2^n/(10n)$ .

- We are interested in explicitly defined Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on *n* variables and take the first with circuit complexity at least  $2^n/(10n)$ .
- To avoid tricks like this one, we say that a function f is explicitly defined if  $f^{-1}(1)$  is in NP.

- We are interested in explicitly defined Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on n variables and take the first with circuit complexity at least  $2^n/(10n)$ .
- To avoid tricks like this one, we say that a function f is explicitly defined if  $f^{-1}(1)$  is in NP.
- Usually, under a Boolean function f we actually understand an infinite sequence {f<sub>n</sub> | n = 1, 2, ... }.

# Known Lower Bounds for Circuits over $B_2$

#### Known Lower Bounds

 $\begin{array}{ll} 2n-c & [Schnorr, 74] \\ 2.5n-o(n) & [Paul, 77] \\ 2.5n-c & [Stockmeyer, 77] \\ 3n-o(n) & [Blum, 84] \end{array}$ 

# Known Lower Bounds for Circuits over $B_2$

#### Known Lower Bounds

 $\begin{array}{ll} 2n-c & [Schnorr, 74] \\ 2.5n-o(n) & [Paul, 77] \\ 2.5n-c & [Stockmeyer, 77] \\ 3n-o(n) & [Blum, 84] \end{array}$ 

#### This Talk

In this talk, we will present a proof of a 7n/3 - c lower bound which is as simple as Schnorr's proof of 2n - c lower bound.

# Known Lower Bounds for Circuits over $B_2$

#### Known Lower Bounds

 $\begin{array}{ll} 2n-c & [Schnorr, 74] \\ 2.5n-o(n) & [Paul, 77] \\ 2.5n-c & [Stockmeyer, 77] \\ 3n-o(n) & [Blum, 84] \end{array}$ 

#### This Talk

In this talk, we will present a proof of a 7n/3 - c lower bound which is as simple as Schnorr's proof of 2n - c lower bound.

#### Gate Elimination

All the proofs are based on the so-called gate elimination method. This is essentially the only known method for proving lower bounds on circuit complexity.

The main idea

The main idea

• Take an optimal circuit for the function in question.

### The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.

### The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.

## Gate Elimination Method

#### The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

## Gate Elimination Method

#### The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

#### Remark

This method is very unlikely to produce nonlinear lower bounds.

#### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

If or all different i, j ∈ {1,..., n}, one obtains at least three different subfunctions by replacing x<sub>i</sub> and x<sub>j</sub> by constants;

### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

- If for all different i, j ∈ {1,..., n}, one obtains at least three different subfunctions by replacing x<sub>i</sub> and x<sub>j</sub> by constants;
- for all *i* ∈ {1,..., *n*}, one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if *n* ≥ 4) by replacing *x<sub>i</sub>* by any constant.

#### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

- If for all different i, j ∈ {1,..., n}, one obtains at least three different subfunctions by replacing x<sub>i</sub> and x<sub>j</sub> by constants;
- for all *i* ∈ {1,..., *n*}, one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if *n* ≥ 4) by replacing *x<sub>i</sub>* by any constant.

### Modular functions

### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

- If for all different i, j ∈ {1,..., n}, one obtains at least three different subfunctions by replacing x<sub>i</sub> and x<sub>j</sub> by constants;
- for all *i* ∈ {1,..., *n*}, one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if *n* ≥ 4) by replacing *x<sub>i</sub>* by any constant.

### Modular functions

• Let 
$$\operatorname{MOD}_{m,r}^n(x_1,\ldots,x_n) = 1 \iff \sum_{i=1}^n x_i \equiv r \pmod{m}$$

### Definition

A function  $f: \{0,1\}^n \to \{0,1\}$  belongs to the class  $Q_{2,3}^n$  if

- If for all different i, j ∈ {1,..., n}, one obtains at least three different subfunctions by replacing x<sub>i</sub> and x<sub>j</sub> by constants;
- for all *i* ∈ {1,..., *n*}, one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if *n* ≥ 4) by replacing *x<sub>i</sub>* by any constant.

### Modular functions

- Let  $MOD_{m,r}^n(x_1,\ldots,x_n) = 1 \iff \sum_{i=1}^n x_i \equiv r \pmod{m}$ .
- Then  $\text{MOD}_{3,r}^n, \text{MOD}_{4,r}^n \in Q_{2,3}^n$ , but  $\text{MOD}_{2,r}^n \notin Q_{2,3}^n$ .

Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

Proof

• Induction on *n*. If  $n \leq 4$ , then the statement is trivial.

Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

- Induction on *n*. If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).

#### Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

- Induction on *n*. If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x<sub>i</sub> and x<sub>j</sub> (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take two values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.

#### Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

- Induction on *n*. If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables x<sub>i</sub> and x<sub>j</sub> (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take two values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.
- Thus, either  $x_i$  or  $x_j$  fans out to another gate P.

#### Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \ge 2n - 8$ .

- Induction on *n*. If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate Q which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take two values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.
- Thus, either  $x_i$  or  $x_j$  fans out to another gate P.
- By assigning this variable, we eliminate at least two gates and get a subfunction from  $Q_{2,3}^{n-1}$ .

#### **Binary functions**

#### **Binary functions**

The set  $B_2$  of all binary functions contains 16 functions f(x, y):

2 constants: 0, 1

### **Binary functions**

- 2 constants: 0, 1
- **2** 4 degenerate functions: x,  $\bar{x}$ , y,  $\bar{y}$ .

### **Binary functions**

- 2 constants: 0, 1
- **2** 4 degenerate functions: x,  $\bar{x}$ , y,  $\bar{y}$ .
- **3** 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .

### **Binary functions**

- 2 constants: 0, 1
- 2 4 degenerate functions: x,  $\bar{x}$ , y,  $\bar{y}$ .
- **3** 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .
- **3** AND-type functions:  $(x \oplus a)(y \oplus b) \oplus c$ , where  $a, b, c \in \{0, 1\}$ .

### **Binary functions**

The set  $B_2$  of all binary functions contains 16 functions f(x, y):

- 2 constants: 0, 1
- 2 4 degenerate functions: x,  $\bar{x}$ , y,  $\bar{y}$ .
- **3** 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .
- **3** AND-type functions:  $(x \oplus a)(y \oplus b) \oplus c$ , where  $a, b, c \in \{0, 1\}$ .

#### Remark

Optimal circuits contain AND- and XOR-type gates only, as constant and degenerate gates can be easily eliminated.

#### AND-type Gates vs XOR-type Gates

• AND-type gates are easier to handle than XOR-type gates.

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, we eliminate not only this gate, but also all its direct successors!

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, we eliminate not only this gate, but also all its direct successors!
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\overline{x}_j$ .

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, we eliminate not only this gate, but also all its direct successors!
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\overline{x}_j$ .
- That is why, in particular, the current record bounds for circuits over  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  are stronger than the bounds over  $B_2$ .

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, we eliminate not only this gate, but also all its direct successors!
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\overline{x}_j$ .
- That is why, in particular, the current record bounds for circuits over  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  are stronger than the bounds over  $B_2$ .
- Usually, the main bottleneck of a proof based on gate elimination is a circuit whose top contains many XOR-type gates.

### Polynomials over GF(2)

• Let  $\tau(f)$  denote the unique polynomial over GF(2) representing f.

- Let  $\tau(f)$  denote the unique polynomial over GF(2) representing f.
- E.g.,  $\tau(MOD_{3,0}^3) = x_1x_2x_3 + (1-x_1)(1-x_2)(1-x_3).$

- Let  $\tau(f)$  denote the unique polynomial over GF(2) representing f.
- E.g.,  $\tau(MOD_{3,0}^3) = x_1x_2x_3 + (1-x_1)(1-x_2)(1-x_3).$
- Note that  $\tau(f)$  is multi-linear.

- Let  $\tau(f)$  denote the unique polynomial over GF(2) representing f.
- E.g.,  $\tau(MOD_{3,0}^3) = x_1x_2x_3 + (1-x_1)(1-x_2)(1-x_3).$
- Note that  $\tau(f)$  is multi-linear.
- It can be easily shown that, for any r,  $\deg(\tau(\text{MOD}_{4,r}^n)) \leq 3$ , while  $\deg(\tau(\text{MOD}_{3,r}^n)) \geq n-1$ .

### Polynomials over GF(2)

- Let  $\tau(f)$  denote the unique polynomial over GF(2) representing f.
- E.g.,  $\tau(MOD_{3,0}^3) = x_1x_2x_3 + (1-x_1)(1-x_2)(1-x_3).$
- Note that  $\tau(f)$  is multi-linear.
- It can be easily shown that, for any r,  $\deg(\tau(\text{MOD}_{4,r}^n)) \leq 3$ , while  $\deg(\tau(\text{MOD}_{3,r}^n)) \geq n-1$ .

#### Lemma (Degree lower bound)

Any circuit computing f contains at least  $deg(\tau(f)) - 1$  AND-type gates.

### Combined Complexity Measure

#### Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance.

### Combined Complexity Measure

#### Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance. Let us increase the weight of a XOR-type gate.

## Combined Complexity Measure

#### Idea

Thus, in a bottleneck case we see only XOR-type gates, however we are given several AND-type gates in advance. Let us increase the weight of a XOR-type gate.

#### Definition

For a circuit C, let A(C) and X(C) denote the number of AND- and XOR-type gates in C, respectively. Let also  $\mu(C) = 3X(C) + 2A(C)$ .

Lemma

For any circuit C computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \ge 6n - 24$ .

Lemma

For any circuit C computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \ge 6n - 24$ .

Proof

Lemma

For any circuit C computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \ge 6n - 24$ .

Proof


• As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate P.

#### Lemma

For any circuit C computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \ge 6n - 24$ .
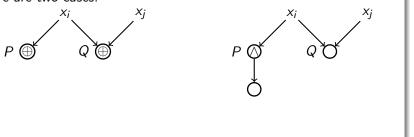
#### Proof

- As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate P.
- There are two cases:




#### Lemma

For any circuit C computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \ge 6n - 24$ .
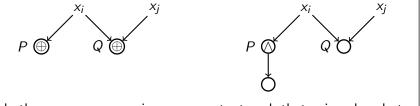
#### Proof

- As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate P.
- There are two cases:



 In both cases, we can assign x<sub>i</sub> a constant such that µ is reduced at least by 6.

### 7n/3 Lower Bound

#### Lemma

Let 
$$f\in Q_{2,3}^n$$
 and  $\deg( au(f))\geq n-c$ , then  $C(f)\geq 7n/3-c'.$ 

### 7n/3 Lower Bound

#### Lemma

Let 
$$f\in Q_{2,3}^n$$
 and  $\deg( au(f))\geq n-c$ , then  $C(f)\geq 7n/3-c'.$ 

#### Proof

Let C be an optimal circuit computing f.

### 7n/3 Lower Bound

#### Lemma

Let 
$$f\in Q_{2,3}^n$$
 and  $\deg( au(f))\geq n-c$ , then  $C(f)\geq 7n/3-c'.$ 

#### Proof

Let C be an optimal circuit computing f.

$$\frac{3X(C)+2A(C) \ge 6n-24}{A(C) \ge n-c-1}$$
$$\frac{A(C) \ge n-c-1}{3C(f)=3X(C)+3A(C) \ge 7n-25-c}$$

 $S_{2^n}$  is the subset of  $B_{n,n}$  (the set of all boolean functions  $f : \{0,1\}^n \to \{0,1\}^n$ ) containing all  $2^n$ ! invertible functions. Any sequence  $f_1, f_2, \ldots$  of functions  $f_i \in S_{2^i}$  — a family of permutations denoted by  $\{f_n\}$ .

 $S_{2^n}$  is the subset of  $B_{n,n}$  (the set of all boolean functions  $f : \{0,1\}^n \to \{0,1\}^n$ ) containing all  $2^n$ ! invertible functions. Any sequence  $f_1, f_2, \ldots$  of functions  $f_i \in S_{2^i}$  — a family of permutations denoted by  $\{f_n\}$ .

Let's consider the following measure of feeble one-wayness:

$$M_F(f_n) = C(f_n^{-1})/C(f_n)$$

 $S_{2^n}$  is the subset of  $B_{n,n}$  (the set of all boolean functions  $f : \{0,1\}^n \to \{0,1\}^n$ ) containing all  $2^n!$  invertible functions. Any sequence  $f_1, f_2, \ldots$  of functions  $f_i \in S_{2^i}$  — a family of permutations denoted by  $\{f_n\}$ . Let's consider the following measure of feeble one-wayness:

$$M_F(f_n) = C(f_n^{-1})/C(f_n)$$

This can be compared with the measure of practical one-wayness:

$$M_P(f_n) = \log_2[C(f_n^{-1})] / \log_2[C(f_n)]$$

A family of permutations  $\{f_n\}$  is said to be feebly-one-way of order k, for some constant k > 1, if

$$C(f_n) = \omega(1)$$
 and  $M_F(f_n) \sim k$ 

A family of permutations  $\{f_n\}$  is said to be feebly-one-way of order k, for some constant k > 1, if

$$C(f_n) = \omega(1)$$
 and  $M_F(f_n) \sim k$ 

A family of permutations  $\{f_n\}$  is said to be practically-one-way of order k, for some constant k > 1, if

$$C(f_n) = \omega(1)$$
 and  $M_P(f_n) \sim k$ 

A family of permutations  $\{f_n\}$  is said to be feebly-one-way of order k, for some constant k > 1, if

$$C(f_n) = \omega(1)$$
 and  $M_F(f_n) \sim k$ 

A family of permutations  $\{f_n\}$  is said to be practically-one-way of order k, for some constant k > 1, if

$$C(f_n) = \omega(1)$$
 and  $M_P(f_n) \sim k$ 

These definitions imply  $C(f_n^{-1}) \sim k \cdot C(f_n)$  and  $C(f_n^{-1}) = [C(f_n)]^{k \pm o(1)}$  respectively.

Let's define  $\phi_n$ , for  $n \ge 3$  as a linear function:

$$\phi_n([x_1,\ldots,x_n])=[y_1,\ldots,y_n]$$

where

$$y_i(x) = x_i \oplus x_{i+1}$$
 for  $i \neq n$   
 $y_n(x) = x_1 \oplus x_{\lceil n/2 \rceil} \oplus x_n$ 

Let's define  $\phi_n$ , for  $n \ge 3$  as a linear function:

$$\phi_n([x_1,\ldots,x_n])=[y_1,\ldots,y_n]$$

where

$$y_i(x) = x_i \oplus x_{i+1}$$
 for  $i \neq n$   
 $y_n(x) = x_1 \oplus x_{\lceil n/2 \rceil} \oplus x_n$ 

The inverse function  $\phi_n^{-1}$  is given by:

$$\begin{aligned} x_i(y) &= (y_1 \oplus \cdots \oplus y_{i-1}) \oplus (y_{\lceil n/2 \rceil} \oplus \cdots \oplus y_n) \qquad i \leq \lceil n/2 \rceil \\ x_i(y) &= (y_1 \oplus \cdots \oplus y_{\lceil n/2 \rceil - 1}) \oplus (y_i \oplus \cdots \oplus y_n) \qquad i > \lceil n/2 \rceil \end{aligned}$$

Theorem

For all  $n \ge 5$ , the functions  $\phi_n$  satisfy

$$C(\phi_n) = n+1$$
 and  $C(\phi_n^{-1}) = \lfloor \frac{3}{2}(n-1) \rfloor$ 

Theorem

For all  $n \ge 5$ , the functions  $\phi_n$  satisfy

$$C(\phi_n) = n+1$$
 and  $C(\phi_n^{-1}) = \lfloor \frac{3}{2}(n-1) \rfloor$ 

Proof

By considering independent realizations of the component function we get C(φ<sub>n</sub>) ≤ n + 1.

Theorem

For all  $n \ge 5$ , the functions  $\phi_n$  satisfy

$$C(\phi_n) = n+1$$
 and  $C(\phi_n^{-1}) = \lfloor \frac{3}{2}(n-1) \rfloor$ 

Proof

- By considering independent realizations of the component function we get C(φ<sub>n</sub>) ≤ n + 1.
- By noticing that each x<sub>i</sub>(y) is a sum of at least [n/2] of the y<sub>k</sub>'s we get C(φ<sub>n</sub>) ≥ L<sup>3</sup>/<sub>2</sub>(n − 1)]

Theorem

For all  $n \ge 5$ , the functions  $\phi_n$  satisfy

$$C(\phi_n) = n+1$$
 and  $C(\phi_n^{-1}) = \lfloor \frac{3}{2}(n-1) \rfloor$ 

Proof

- By considering independent realizations of the component function we get C(φ<sub>n</sub>) ≤ n + 1.
- By noticing that each x<sub>i</sub>(y) is a sum of at least [n/2] of the y<sub>k</sub>'s we get C(φ<sub>n</sub>) ≥ L<sup>3</sup><sub>2</sub>(n − 1)]
- It can be easily verified that the previous two bounds are exact.

### Nonlinear family with feeble one-wayness of order 2

#### Remark

It is easy to modify the previous family to make it one-way of order 2 (still being linear). However, it is even simipler to construct a non-linear family.

#### Construction

The family  $\nu_n$  results from composition  $\beta_n(\alpha_n(x))$  of linear permutation  $\alpha_n([x_1, \ldots, x_n]) = (z_1, \ldots, z_n)$  with a nonlinear permutation  $\beta_n([z_1, \ldots, z_n]) = (y_1, \ldots, y_n)$ , where:

$$z_i(x) = x_i \oplus x_{i+1} \quad \text{for } i \neq n; \quad z_n(x) = x_n$$
$$y_i(z) = z_i \quad \text{for } i \neq n; \quad y_n(z) = z_n \oplus [\overline{(z_1 \oplus \dots \oplus z_{n-2})} \land z_{n-1}]$$

### Nonlinear family with feeble one-wayness of order 2

#### Construction

The inverse permutations  $\beta_n^{-1}([y_1, \dots, y_n]) = (z_1, \dots, z_n)$  and  $\alpha_n^{-1}([z_1, \dots, z_n]) = (x_1, \dots, x_n)$  will be:  $z_i(y) = y_i$  for  $i \neq n$ ;  $z_n(y) = y_n \oplus [\overline{(y_1 \oplus \dots \oplus y_{n-2})} \land y_{n-1}]$  $x_i(z) = z_i \oplus \dots \oplus z_n$  for  $i \neq n$ ;  $x_n(z) = z_n$ 

### Nonlinear family with feeble one-wayness of order 2

#### Construction

The composition of  $\alpha_n$  and  $\beta_n$  yields  $\nu_n(x) = \beta_n(\alpha_n(x))[y_1, \ldots, y_n]$ , and  $\nu_n^{-1}(y) = \alpha_n^{-1}(\beta_n^{-1}(y)) = [x_1, \ldots, x_n]$  where:

$$y_{i}(x) = x_{i} \oplus x_{i+1} \quad \text{for } i \neq n; \quad y_{n}(x) = x_{n} \oplus [\overline{(x_{1} \oplus x_{n-1})} \land (x_{n-1} \oplus x_{n})]$$
$$x_{i}(y) = (y_{i} \oplus \dots \oplus y_{n}) \oplus [\overline{(y_{1} \oplus \dots \oplus y_{n-2})} \land y_{n-1}] \quad \text{for } i \neq n$$
$$x_{n}(y) = y_{n} \oplus [\overline{(y_{1} \oplus \dots \oplus y_{n-2})} \land y_{n-1}]$$

#### Theorem

For all  $n \ge 4$ , the functions  $\nu_n$  satisfy

$$C(\nu_n) = n + 2$$
 and  $C(\nu_n^{-1}) = 2(n-1)$ 

### Conclusion

• The results described in the first two sections of this talk were obtained together with Alexander S. Kulikov and Arist Kojevnikov.

### Conclusion

- The results described in the first two sections of this talk were obtained together with Alexander S. Kulikov and Arist Kojevnikov.
- Now we are working on improving the results of the last section (obtained by Alain Hiltgen) together with my advisor Edward A. Hirsch.

### Conclusion

- The results described in the first two sections of this talk were obtained together with Alexander S. Kulikov and Arist Kojevnikov.
- Now we are working on improving the results of the last section (obtained by Alain Hiltgen) together with my advisor Edward A. Hirsch.
- It is not easy to improve the constant 2 in the last section, because you need to prove a nontrivial lower bound to do this.

# Thank you for your attention!